

1 percent dimming with wide LED voltage and an integrated LLC transformer

Board sales name: REF-ICL5102-U130W-CC

Author: Yi Wang



About this document

Scope and purpose

ICL5102 is an integrated combo controller IC aimed to control and drive the boost PFC + resonant half-bridge (HB) topology (LLC/LCC) combined. The superior performance of its THD optimizer makes it very suitable for applications with stringent requirements on the input power quality, such as LED lighting. Infineon's proprietary coreless transformer-based high-side (HS) MOSFET driver enables a robust and efficient HB drive at high operating frequency up to 500 kHz in the steady-state.

This work reports the experimental results of a 130 W PFC + LLC LED driver design based on our ICL5102 controller and cost-effective 650 V MOSFETs of the P7 series. Key performance of this board:

- 1. An integrated LLC transformer design
- 2. 93 percent system efficiency at full power, 230 V_{RMS} and 50 Hz
- 3. 1 percent analog dimming in a wide LED voltage range (38~76 V)
- 4. Excellent power quality
 - a. THD < 10 percent for load > 10 percent power at 267 V_{RMS} and 50 Hz
 - b. PF > 0.9 for load > 20 percent power at 267 V_{RMS} and 50 Hz
 - c. Harmonics fulfilling IEC61000-3-2 class C edition 5.1 above 10 percent load

Intended audience

This document is intended for technical experts who intend to use this ICL5102 demonstration board, either for ICL5102 functional tests, or as a reference for an ICL5102-based product development.

Engineering Report



1 percent dimming with wide LED voltage and an integrated LLC transformer

Table of contents

Table of contents

Abou	ut this document	
Table	le of contents	
1	IC introduction	3
2	Board description	4
2.1	Electrical specification	
2.2	Schematics and layouts	6
2.3	Board setup	10
3	Electrical performance	11
3.1	System performance	
3.2	Steady-state waveforms	13
3.3	Start-up behavior	14
3.4	Load transient	15
3.5	Protections	16
3.5.1	Brown-out protection	16
3.5.2	Open load protection	16
4	Thermal performance	17
5	EMI performance	18
6	Datasheets of magnetic components	19
7	Bill of materials	
David	ision history	27





IC introduction

1 IC introduction

ICL5102 is an integrated combo IC designed to drive and control the boost PFC + resonant HB topology (LLC/LCC) in combination. The normal voltage version (650 V max.) can cover the applications with universal mains up to $305 \, V_{RMS}$, while its high-voltage version, ICL5102HV, can handle $980 \, V$ (max. value) on the HB driver part, which is suited to horticultural lighting applications and other industrial applications where the input mains voltage is up to $530 \, V_{RMS}$.

The pin maps of ICL5102 and ICL5102HV are given in Figure 1. Thanks to Infineon's proprietary coreless transformer technology, ICL5102/HV's high-side MOSFET driver is very robust against dV/dt and negative voltage peak on the switch node of the half bridge, and it is very efficient at high operating frequency.

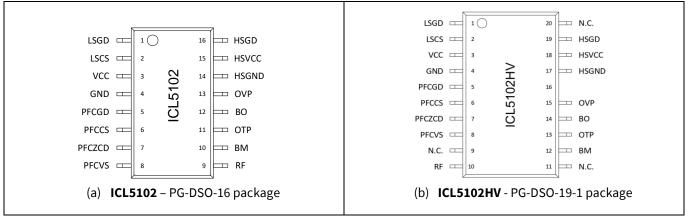


Figure 1 Pin maps of (a) ICL5102 and (b) ICL5102HV

The other key features of ICL5102 are summarized as follows:

Key features:

- Integrated two-stage combo controller allowing for reduced number of external components, optimized bill of materials (BOM) and form factor.
- Maximum **500 kHz** HB switching frequency in continuous operation and soft-start frequency up to 1.3 MHz.
- THD optimization ensuring best-class THD performance and low harmonic distortion at light load. Easy to pass IEC61000-3-2 class C edition 5.1.
- PFC controller with critical conduction mode (CrCM) and discontinuous conduction mode (DCM).
- Resonant HB controller with fixed or variable switching frequency control.
- Burst mode supporting the standby mode with low power consumption (<500 mW, system level).
- Supports universal AC input voltage and excellent system efficiency.

Protection coverage:

- Input brown-out protection
- PFC bus overvoltage protection (OVP)
- PFC overcurrent protection (OCP)
- Output OVP, OCP/short-circuit protection
- Output overpower/overload protection (OPP)
- Half-bridge capacitive mode protection
- Overtemperature protection (OTP)



infineon

Board description

2 Board description

This 130 W demonstration board has been designed to show the great power quality of an ICL5102-based PFC+LLC converter for LED lighting application. A possibility of 1 percent analog dimming of an LLC toplogy with a wide LED output range is also demonstrated with an integrated and compact LLC transformer. Here, the 1 percent dimming is realized without entering the burst mode and hence, a great light quality is guaranteed to fulfill the more and more stringent requirements of temporal light artifacts (TLA), such as LED current modulation limitation in IEEE1789 recommendation, and the stroboscopic visibility measure (SVM) and P_{st}^{LM} limitation in the EU single lighting regulation.

The main characteristics of this demonstration board are summarized below:

- 1. An integrated LLC transformer designed for size and cost reduction
- 2. 93 percent system efficiency at 130 W, 230 V_{RMS}, 50 Hz
- 3. 1 percent analog dimming in a wide LED voltage range (38~76 V), without entering the burst mode
- 4. Excellent power quality
 - a. THD < 10 percent for load > 10 percent power at 267 V_{RMS} , 50 Hz
 - b. PF > 0.9 for load > 20 percent power at 267 V_{RMS} , 50 Hz
 - c. Harmonics fulfilling IEC61000-3-2 class C edition 5.1 above 10 percent load
- 5. Infineon's cost-effective P7 series MOSFETs are used for both PFC and LLC stages.

2.1 Electrical specification

This LED driver is designed to have a rectangular output window, which is shown in **Figure 2**. The driver can be dimmed down via an easy-to-use 0-10 V analog dimming interface. At 10 V dimming voltage, the output is supposed to provide approximately 1.71 A within the given output LED voltage range. With 38 V LED voltage, the driver can generate 1.3 W output power at very low dimming voltage.

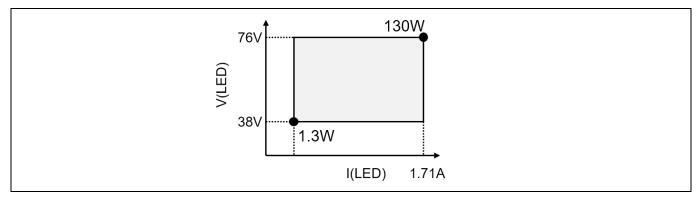


Figure 2 Output operating window

Table 1 lists the key electrical specifications of this demo board.

Table 1 Key electrical specifications

Item	Symbol	Min.	Тур.	Max.	Unit	Remarks
AC input voltage	$V_{in.ac}$	90	_	267	V_{RMS}	
Brown-out voltage	V _{in.BO}	-	83	-	V_{RMS}	Tested 50 Hz mains
Brown-in voltage	$V_{in.BI}$	_	90	-	V_{RMS}	Tested 50 Hz mains
Input frequency	f _{in}	47	_	63	Hz	
Efficiency	η	_	93	-	_	100 percent load
			percent			at 230 V _{RMS} , 50 Hz



${\bf 1} \ {\bf percent} \ {\bf dimming} \ {\bf with} \ {\bf wide} \ {\bf LED} \ {\bf voltage} \ {\bf and} \ {\bf an} \ {\bf integrated} \ {\bf LLC} \ {\bf transformer}$

Item	Symbol	Min.	Тур.	Max.	Unit	Remarks
Rated LED voltage	V _{LED}	38	_	76	V	
LED current range	I _{LED}	0.017	_	1.72	А	
LED power	P _{LED}	-	_	130	W	
Analog dimming voltage	V _{DIM}	0	_	10	V	
LLC frequency range	f _{LLC}	35*	_	65**	kHz	*V _{LED} = 76 V, V _{DIM} = 10 V
						$**V_{LED} = 38 \text{ V}, V_{DIM} = 0.1 \text{ V}$
Total harmonic distortion	THD	-	_	10	percent	Greater than 10 percent load at 267 V _{RMS} , 50 Hz
Power factor	PF	0.9	_	_		Greater than 20 percent load
Time-to-light	T2L			0.5	S	
EMI		1	EN 55015			Tested at full load and half load
Harmonics	E	EN 61000-3-	·2 class C, e	edition 5.1		Greater than 10 percent load at 230 V _{RMS} , 50 Hz



${\bf 1}~{\bf percent~dimming~with~wide~LED~voltage~and~an~integrated~LLC~transformer}$

Board description

2.2 Schematics and layouts

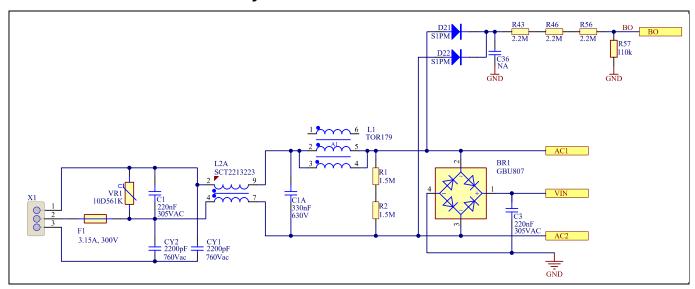


Figure 3 Schematic of the input EMI filter and the brown-out sensing network

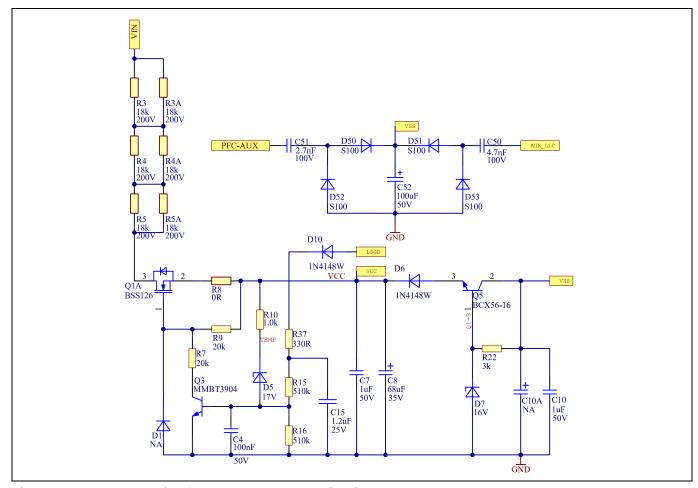


Figure 4 Schematic of the start-up and V_{cc} circuit



1 percent dimming with wide LED voltage and an integrated LLC transformer

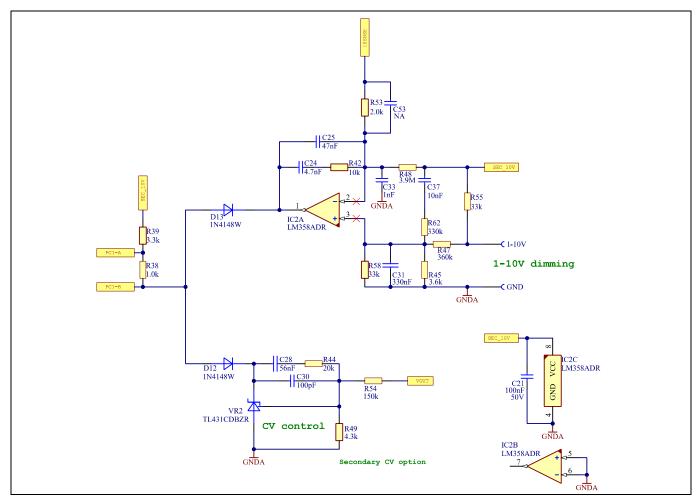


Figure 5 Schematic of the secondary-side control circuit





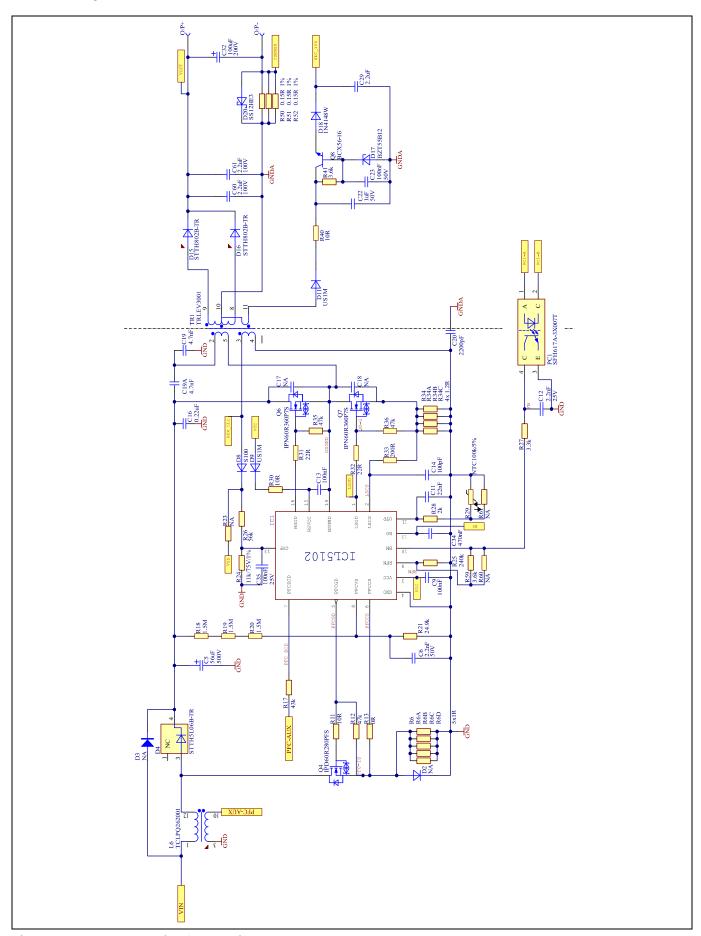


Figure 6 Schematic of the main power stage



1 percent dimming with wide LED voltage and an integrated LLC transformer

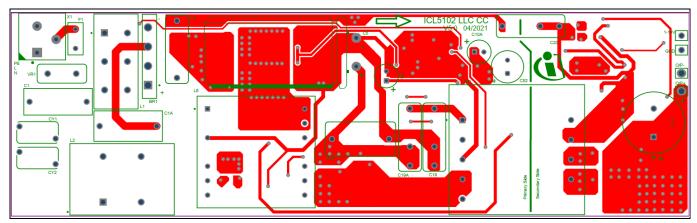


Figure 7 Layout of the through-hole component side

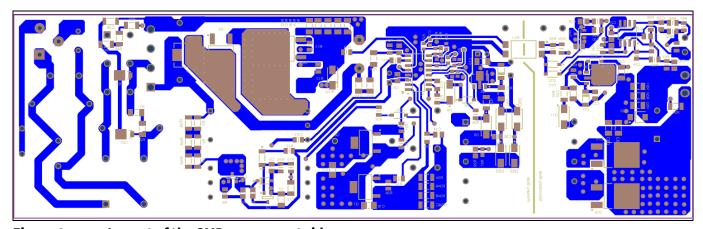


Figure 8 Layout of the SMD component side





Board description

2.3 Board setup

This 18 cm long board has a two-sided PCB with 2 oz. (70 μ m) copper thickness. An external DC voltage supply (the maximum output voltage is at least 10 V and output current rating is at least 100 mA) should be connected to the LED side for dimming.

Here, the PFC inductor is the size of a PQ2625 core set and the integrated LLC transformer uses a special EV30 core set, which is 5 mm longer in total than a standard EVD25 core.

The PCB and its connectors are indicated in Figure 9a. Please pay attention to the connector polarities.

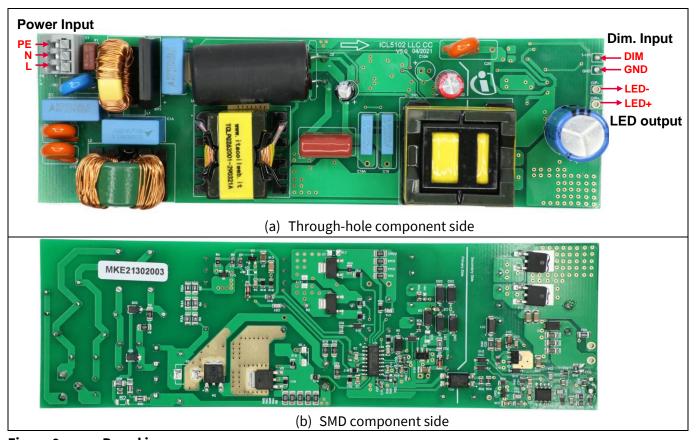


Figure 9 Board images





Electrical performance

3 Electrical performance

The electrical performance of this board is shown below, in the aspects of:

- System performance (LED current dimming curve, system efficiency, THD, power factor and input current harmonics)
- Steady-state waveforms
- Start-up behavior
- Load transient behavior
- Protection behavior (brown-out protection, output OVP)

3.1 System performance

Figure 10 shows the measured LED current curve with the dimming voltage. These curves are pretty linear all the way down to 0.1 V.

Figure 11 illustrates the system efficiency from 100 percent to 1 percent load. At full load with 230 V_{RMS} input, the efficiency is around 93 percent, and this value comes to about 91.4 percent when input is 120 V_{RMS} . The efficiency measurement is done after the driver has been thermally stabilized.

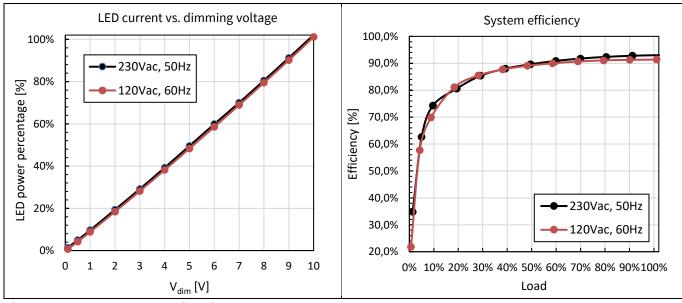


Figure 10 LED current vs. dimming voltage (V_{LED} = 76 V)

Figure 11 System efficiency vs. load (V_{LED} = 76 V)

Figure 12 presents the input power factor with the LED load. It shows that even at the mains conditions of 277 V AC, 60 Hz (which is beyond our board specification), the board can still achieve greater than 0.9 power factor above 30 percent load. At 267 V AC and 50 Hz, power factor of greater than 0.9 is possible for loads above 20 percent.

The excellent power quality of this board can also be seen from the THD performance. **Figure 13** provides the measured THD result at various load and input voltage conditions. It can be seen that the THD is smaller than 10 percent at load greater than 10 percent over the full input ranges.

Figure 14 and **Figure 15** show the input current harmonics results at full load and 10 W load. Both fulfill the requirements of IEC61000-3-2 class C, edition 5.1.





Electrical performance

The excellent input power quality is the result of of the EMI filter and the THD optimizer function within ICL5102.

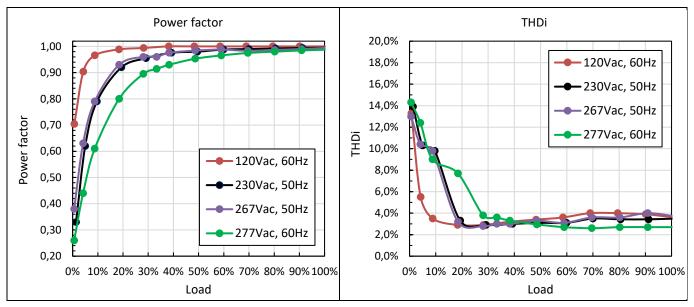


Figure 12 Power factor vs. load

Figure 13 THD vs. load

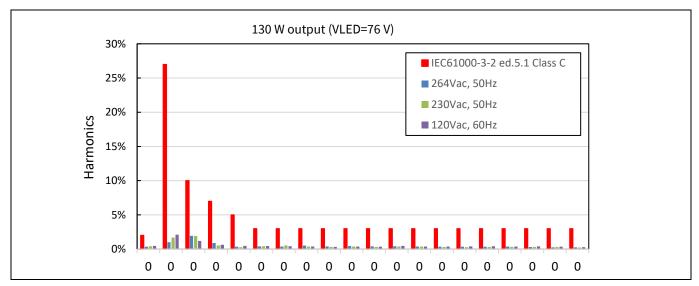


Figure 14 Input current harmonics at 130 W load





Electrical performance

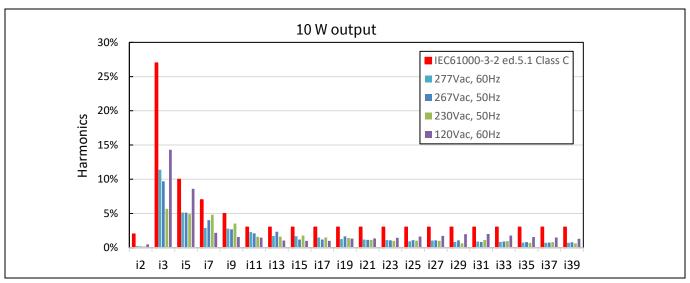


Figure 15 Input current harmonics at 10 W load

3.2 Steady-state waveforms

The key waveforms at various input voltages, and at full load and 1 percent load, are shown in **Figure 16** to **Figure 19**. In each measurement of these figures, the number of LEDs in series is the same, but the LED current drives the LED voltage differently due to the dynamic resistance.

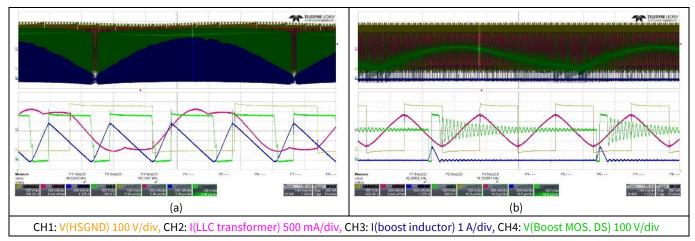


Figure 16 Boost and LLC waveforms at 230 V_{RMS} (a) $V_{dim} = 10 V$, $V_{LED} = 76 V$ and (b) $V_{dim} = 0.1 V$, $V_{LED} = 65 V$

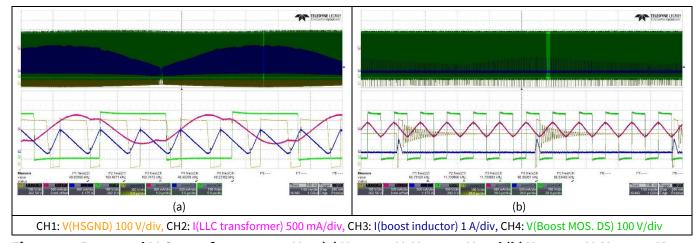


Figure 17 Boost and LLC waveforms at 230 V_{RMS} (a) $V_{dim} = 10 V$, $V_{LED} = 46 V$ and (b) $V_{dim} = 0.1 V$, $V_{LED} = 39 V$



1 percent dimming with wide LED voltage and an integrated LLC transformer

Electrical performance

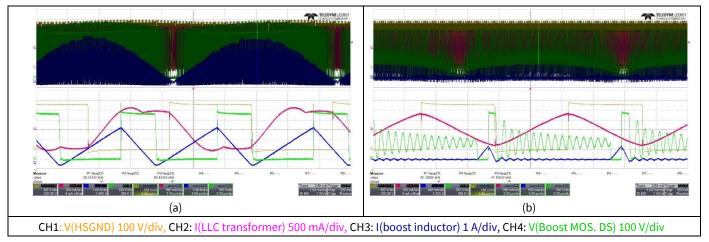


Figure 18 Boost and LLC waveforms at 120 V_{RMS} (a) $V_{dim} = 10 V$, $V_{LED} = 76 V$ and (b) $V_{dim} = 0.1 V$, $V_{LED} = 65 V$

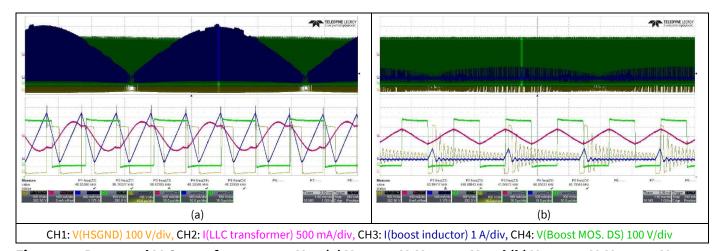


Figure 19 Boost and LLC waveforms at 120 V_{RMS} (a) $V_{dim} = 10 V$, $V_{LED} = 46 V$ and (b) $V_{dim} = 0.1 V$, $V_{LED} = 39 V$

3.3 Start-up behavior

The start-up behavior of the V_{CC} voltage, LED current, etc. at various input voltages, LED voltages and dimming voltages are recorded via **Figure 20 (a to d)**. Here, the time-to-light (less than 0.5 s) can be observed from the V_{CC} ramping up to the LED current ramping up.





Electrical performance

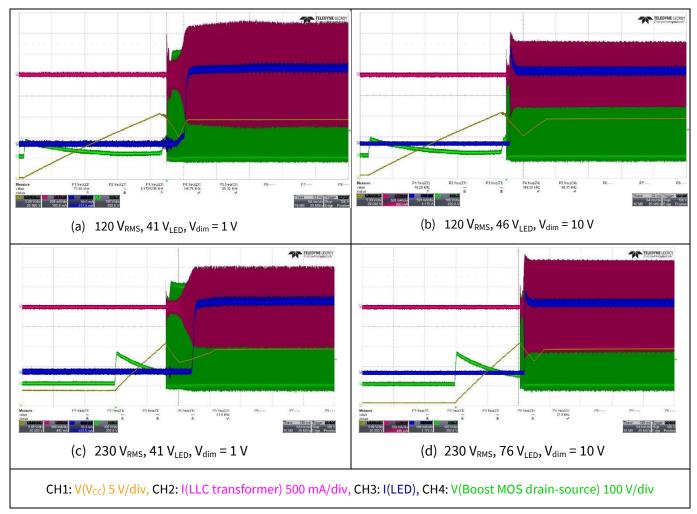


Figure 20 Start-up behavior of the V_{cc}, LED current, LLC transformer current at different operating conditions (a to d)

3.4 Load transient

Figure 21 shows the LED current transient when the dimming voltage jumps from 0.1 V to 10 V in 6 ms. The LED current ramps up smoothly.

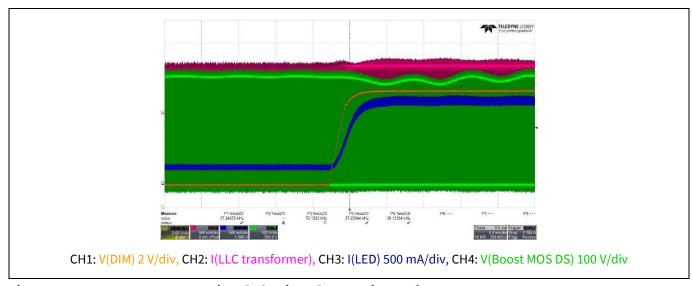


Figure 21 LED current transient behavior when V_{dim} jumps from 0.1 V to 10 V





Electrical performance

Protections 3.5

3.5.1 **Brown-out protection**

The external resistors and capacitors around the brown-out pin are tuned such that the brown-out protection is triggered around 83 V_{RMS} and brown-in around 90 V_{RMS}.

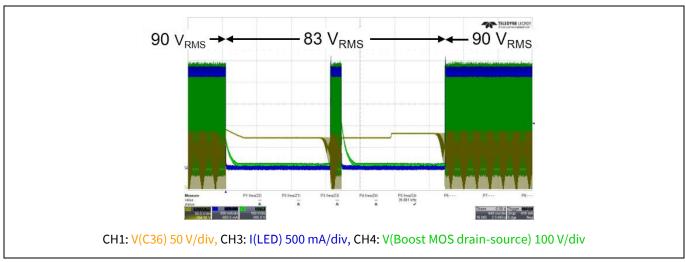


Figure 22 Brown-out protection (brown-out point at 83 V_{RMS})

3.5.2 **Open load protection**

The OVP pin is used for output overvoltage protection. Figure 23 shows the waveforms when the LED load is disconnected and the OVP function shuts down the IC once the overvoltage is detected. During the OVP phase, the external start-up circuit is activated repeatedly but the overall system average power consumption is kept below 0.4 W.

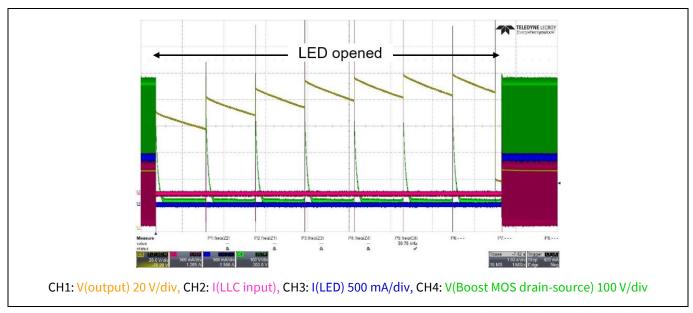


Figure 23 **LED** open protection





Thermal performance

4 Thermal performance

The temperature profiles of this open-frame board at $120 \, V_{RMS}$ and $230 \, V_{RMS}$, full load are presented in **Figure 24** and **Figure 25**. The room temperature is 22° C. It can be found that the output diodes and the LLC transformer are around 80° C in the worst case. Here, the copper plane area of the output diodes can be extended for further cooling. The hottest component is the rectifier diode bridge (86° C) at $120 \, V_{RMS}$ input and $130 \, W$ output power. A diode bridge with higher current rating and better cooling package can be used to bring down its temperature rise.

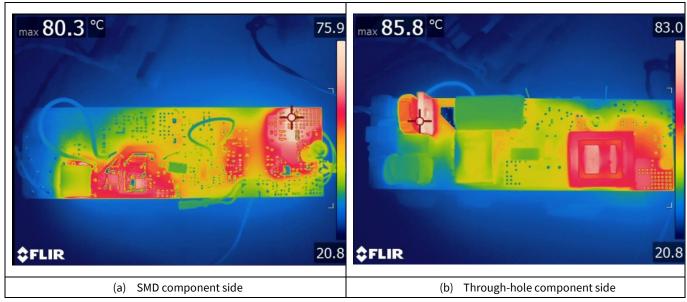


Figure 24 Infrared images at 120 V_{RMS}, 76 V LED and 130 W

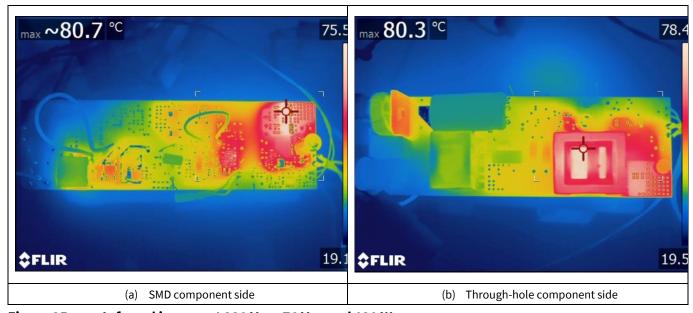


Figure 25 Infrared images at 230 V_{RMS}, 76 V_{LED} and 130 W





EMI performance

5 EMI performance

The conducted EMI performance (9 kHz to 30 MHz) has been measured at 230 V_{RMS} input with full (**Figure 26**). Note that these tests are conducted with this open-frame board and with its protective earth connected to the earth of the LISN.

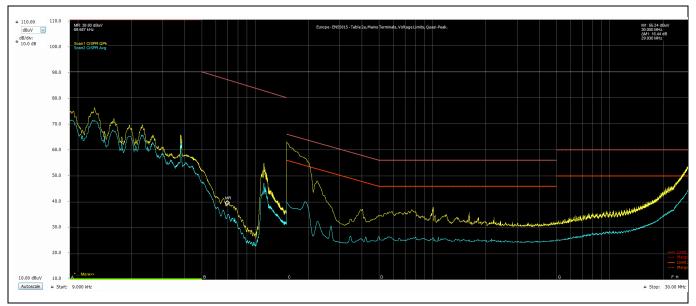


Figure 26 Conducted EMI at 230 V_{RMS} input and 130 W output





Datasheets of magnetic components

6 Datasheets of magnetic components

The datasheets of all magnetic components are shown below.

	itacoil [®]	nh	DATASHEET		12/	/10/2020	REV	<u>'</u>		00
	Itaconv	VED	EDITED		Dav	vide Maida	APP	ROVED		Dario Radaelli
FINA	AL P/N	SCT22132	23	REV	00	SAMPLING CODE	SCT	2213223-19.0	394	
PREL	PRELIMINARY P/N OP201001	10012		00	CUSTOMER P/N					
CUST	TOMER	INFINEON	TECHNOLOGI	ES AG (N	Munich)				
D.F.C.						22 11 2 2 4				
	CRIPTION		Common mod	ie induct	tor 2 x	22mH 2,3A				
	//FEATURES		1			0.101/11 10	,			
	ctance L1	1.4	>15,4mH			@10KHz 10			10.1	1
	age Inductance	L1	147uH typ			@100KHz 1	V		L2 shorte	ed
	L1=L2		185mΩ typ							
	ninal current		2,3A							
	ns rated voltage		250V							
	s Ratio L1:L2		1:1			4.510.4011				
Diele	ectric Strenght		L1/L2			1,5KV/2"				
LATO	OUT (bottom vie	°.	5 0 L2	WING			B	→ H		Y • • • • • X
LATO	1 0 L1 0	°.	5 •	WING			B	H L		Y • X • X
		°.	5 •	WING			B	H H		Y • X • V
	1 0 L1 10 ENSIONS (mm) 27,4 max	°.	5 •	WING	H 3	0,9 max	B	12,0 typ	x	Y X X 10,0 typ
DIMI	1 0 L1 10 ENSIONS (mm)	°	5 • L2 •	WING	H 3	0,9 max	B		x	Y X X 10,0 typ
DIMI A L	1 0 L1 10 ENSIONS (mm) 27,4 max 3,5 min	O	5 • L2 • 6	WING	H 3	0,9 max	В		X	Y X X 10,0 typ
DIMI A L NOTI ROHS REAC	1 10 ENSIONS (mm) 27,4 max 3,5 min ES S compliant [Dir CH compliant [R	B D Dectives 20: egulation (institutes your a	18,7 max 1,0 typ	2015/86] see htt	3/EU] : tps://w	0,9 max see https://www.itww.itacoilweb.com forth in the Disclaimer at 1	acoilw n/regu	12,0 typ eb.com/files/ latory-compli	RoHS.pdf	Y X X 10,0 typ

Figure 27 Common mode EMI choke - L2A



1 percent dimming with wide LED voltage and an integrated LLC transformer

Datasheets of magnetic components

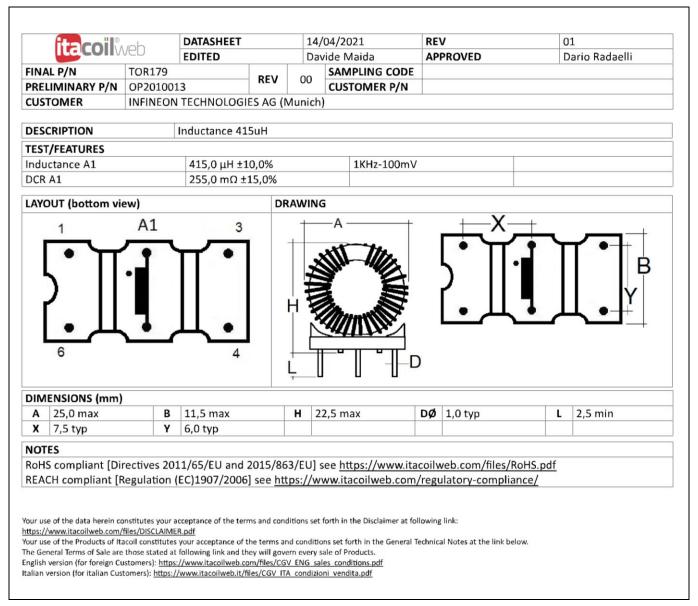


Figure 28 Differential mode EMI choke - L1



1 percent dimming with wide LED voltage and an integrated LLC transformer

Datasheets of magnetic components

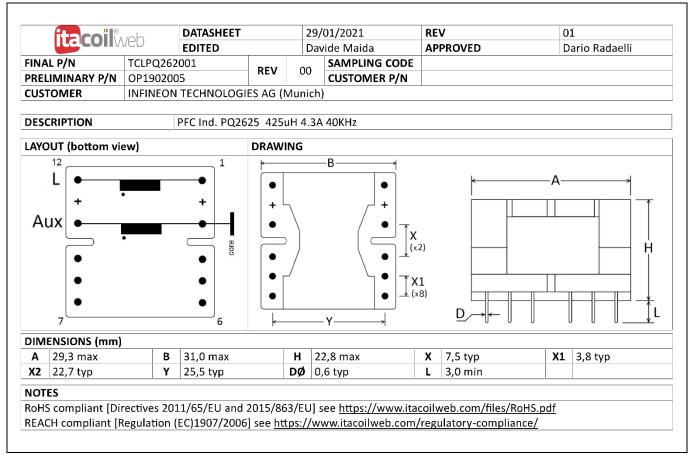


Figure 29 Boost inductor - L6



1 percent dimming with wide LED voltage and an integrated LLC transformer

Datasheets of magnetic components

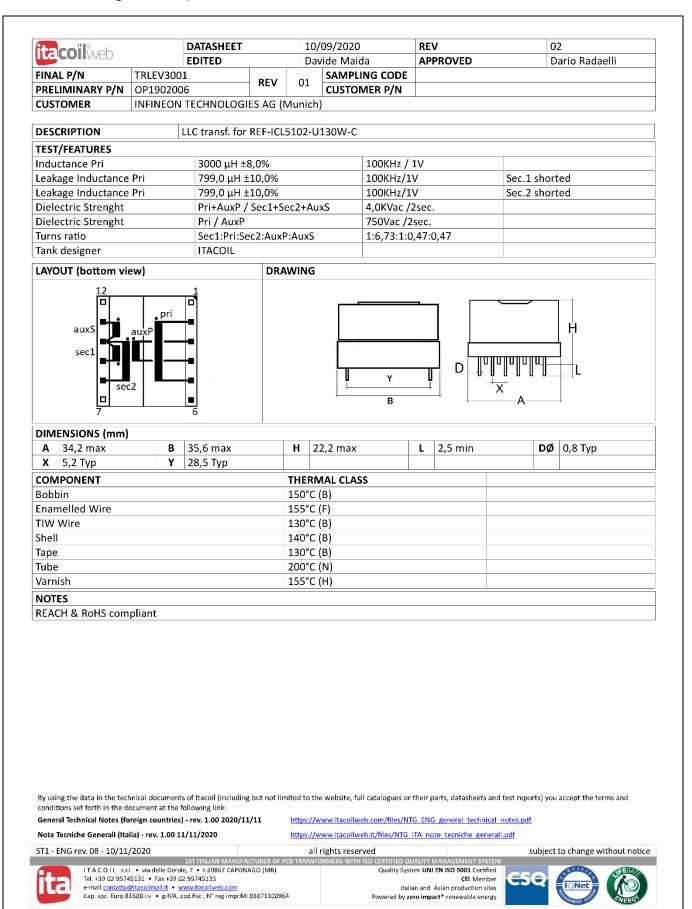


Figure 30 Integrated LLC transformer - TR1



1 percent dimming with wide LED voltage and an integrated LLC transformer Bill of materials

Qty	Designator	Description	Manufacturer	MPN	
1	1 to 10 V	Violet cable/CON-F-THT-SSW-101-02-S-S	Manufacturer		
1	BR1	GBU807/1000 V/SIP-4	Taiwan	GBU807	
			Semiconductor		
2	C1, C3	Capacitor 220 nF/305 V AC/radial type/10%	Epcos	B32922C3224K	
1	C1A	Capacitor 330 nF/630 V/radial type/20%	TDK Corporation	B32922C3334M189	
5	C4, C9,	Capacitor 100 n/50 V/0805/X7R/10%	TDK	C2012X7R1H104K085AA	
	C13, C21,				
	C23				
1	C5	Capacitor 56 μ/500 V/	Nichicon	UCY2H560MHD	
		CAPPR750D80D1825H2700/20%			
1	C6	Capacitor 2.2 n/50 V/0805/X7R/10%	KEMET	C0805C222K5RACTU	
1	C7, C10	Capacitor 1 μ/50 V/1206/X7R/10%	TDK	C3216X7R1H105K160AB	
1	C8	Capacitor 68 μ/35 V/	Panasonic	EEUFR1V680	
		CAPPRD250W50D630H1220B/20%			
1	C11	Capacitor 22 n/50 V/0603/X7R/5%	Murata	GRM188R71H223JA01	
1	C12	Capacitor 2.2 n/25 V/0603/C0G/5%	KEMET	C0603C222J3GACTU	
1	C14	Capacitor 100 p/50 V DC/0805/C0G (EIA)/5%	Murata	GCM2165C1H101JA16#	
1	C15	Capacitor 1.2 μF/25 V/1206/X7R/10%	AVX	12063C224K4Z2A	
1	C16	Capacitor 220 n/630 V DC/	Panasonic	ECQE6224JF	
		CAPRR1500W80L1850T900H1750B/5%		_	
2	C19, C19A	Capacitor 4.7 n/1600 V/	TDK	B32671L0472J000	
		CAPRR1000W60L1300T600H1200B/5%			
1	C20	Capacitor 2200 p/760 V AC/disk/pitch 10 to	Vishay	440LD22-R	
		15/Y5U/20%	,		
1	C22	Capacitor 1 μ/50 V/1206/X7R/10%	TDK	C3216X7R1H105K160AB	
1	C24	Capacitor 4.7 n/50 V/0805/C0G/5%	Murata	GRM2165C1H472JA01	
1	C25	Capacitor 47 nF/50 V/0805/X7R/10%	Murata	GRM21BR71H473KA01	
1	C28	Capacitor 56 n/50 V/0805/X7R/10%	Kemet	C0805C563K5RACTU	
1	C29	Capacitor 2.2 μF/25 V/1206/X7R/10%	Murata	GCM31MR71E225KA57	
1	C30	Capacitor 100 p/50 V DC/0805/C0G (EIA)/5%	Murata	GCM2165C1H101JA16#	
1	C31	Capacitor 330 n/50 V/0805/X7R/10%	AVX	08055C334K4Z2A	
1	C32	Capacitor 100 μF/200 V/	Vishay	MAL215262101E3	
		CAPPRD750W80D1625H1220B/20%	,		
1	C33	Capacitor 1 n/50 V DC/0805/C0G (EIA)/5%	Murata	GCM2195C1H102JA16#	
1	C34	Capacitor 470 nF/25 V/0603/X5R/10%	Murata	GRM188R61E474KA12	
1	C35	Capacitor 100 n/25 V/0603/X7R/10%	KEMET	C0603C104K3RAC	
1	C37	Capacitor 10 n/50 V DC/0805/C0G (EIA)/5%	Murata	GCM21B5C1H103JA16#	
1	C50	Capacitor 4.7 nF/100 V/0805/X7R/10%	Murata	GRM216R72A472KAC4	
1	C51	Capacitor 2.7 nF/100 V/0805/C0G/5%	Murata	GRM2165C2A272JA01	
1	C52	Capacitor 100 μF/50 V/WCAP-	Würth Elektronik		
		ATG8_D8H11.5			
1	C60	Capacitor 2.2 μ/100 V/1206/X7R/10%	Murata	GRM31CR72A225KA73	
1	C61	Capacitor 2.2 μ/100 V/1206/X7R/10%	Murata	GRM31CR72A225KA73	
2	CY1, CY2	Capacitor 2200 p/760 V AC/	Vishay	440LD22-R	
_	, -·-	CAPRR950W81L1090T570H1410B/Y5U/20%	, ,)	
1	D4	STTH5L06B-TR/30 V/DPAK-3	STMicroelectronics	STTH5L06B-TR	



1 percent dimming with wide LED voltage and an integrated LLC transformer

1	D5	Diode 17 V/SOD-80C	Nexperia	TZM5247B-GS08CT
1	D6	1N4148W/100 V/SOD-123	Diodes	1N4148W-7-F
	D0	1114140W/100 V/3OD-123	Incorporated	11/4140//-1-1
1	D7	TZMB16/16 V/SOD-80C	Vishay	TZM5246B-GS18
5	D8, D50,	\$100/100 V/DO-214AC (SMA)	Onsemi	S100
3		3100/100 V/DO-214AC (SMA)	Onsemi	3100
	D51, D52, D53			
	+	LIC1M/1000 V/DO 21 4AC (CMA)	Violence.	LICIM FO/CIT
	D9, D11	US1M/1000 V/DO-214AC (SMA)	Vishay	US1M-E3/61T
4	D10, D12,	1N4148W/100 V/SOD-123	Diodes	1N4148W-7-F
	D13, D18	D: L CTTUCCOD TD/DDAY	Incorporated	CTTUOGGD TD
1	D15	Diode STTH802B-TR/DPAK	STMicroelectronics	
1	D16	Diode STTH802B-TR/DPAK	STMicroelectronics	STTH802B-TR
1	D17	BZT55B12/12 V/SOD-80C	Vishay	BZT55B12
1	D20	SS12HE3/20 V/DO-214AC	Vishay	SS12HE3_A/H
2	D21, D22	S1PM/1 kV/DO-220AA	Vishay	S1PM-M3/84A
1	F1	3.15 A/300 V/	Littelfuse	36913150000
		FUSRR508W60L850T400H800B/		
1	Glue pad	Glue pad	3M	4016-1/2"x36yd
1	GND	Gray cable/CON-F-THT-SSW-101-02-S-S	Manufacturer	
1	Heat shrink	Heat shrink	e.g., Alpha Wire	
1	IC1	ICL5102/PG-DSO-16	Infineon	ICL5102
1	IC2	LM358ADR/SOIC-8	Texas Instruments	LM358ADR
1	L1	Inductor 415 μH/THT	Itacoil	TOR179
1	L2	Inductor 44 mH/THT	Itacoil	SCT2213223
1	L6	Inductor 425 μH/THT	Itacoil	TCLPQ262001
1	O/P-	Black cable/CON-F-THT-SSW-101-02-S-S	Manufacturer	
1	O/P+	Red cable/CON-F-THT-SSW-101-02-S-S	Manufacturer	
1	PC1	SFH617A-3X007T/SMD-4,	Vishay	SFH617A-3X007T
		1016LS254P650W458L440H		
		10102323 11 03000 1302 1 1011		
	PCB	PCB		
1 1	+		Infineon	BSS126
	Q1A	PCB	Infineon NXP	BSS126 MMBT3904,215
1	+	PCB BSS126/PG-SOT-23-3-5		
1	Q1A Q3	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3	NXP	
1 1 1	Q1A Q3 Q4	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3	NXP Semiconductors	MMBT3904,215
1 1 1 1	Q1A Q3 Q4 Q5	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89	NXP Semiconductors Infineon	MMBT3904,215 IPD60R280P7S BCX56-16
1 1 1 1 2	Q1A Q3 Q4 Q5 Q6, Q7	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223	NXP Semiconductors Infineon NXP	MMBT3904,215 IPD60R280P7S
1 1 1 2 1	Q1A Q3 Q4 Q5 Q6, Q7 Q8	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89	NXP Semiconductors Infineon NXP Infineon NXP	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16
1 1 1 2 1 2	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L
1 1 1 2 1	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A,	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89	NXP Semiconductors Infineon NXP Infineon NXP	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16
1 1 1 2 1 2	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A,	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A	PCB BS\$126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK
1 1 1 2 1 2	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A R6, R6A, R6B, R6C,	PCB BS\$126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A R6, R6A, R6B, R6C, R6D	PCB BS\$126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1% Resistor 1R0/200 V/1206/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay Panasonic	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK ERJ8RQF1R0 V
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A R6, R6A, R6B, R6C, R6D	PCB BSS126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1% Resistor 20k/150 V/0805/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay Panasonic Yageo/Phycomp	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK ERJ8RQF1R0 V RC0805FR-0720K
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A R6, R6A, R6B, R6C, R6D R7, R9 R8, R13	PCB BS\$126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1% Resistor 1R0/200 V/1206/1% Resistor 0 R/150 V/0805/1% Resistor 0 R/150 V/0805/	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay Panasonic Yageo/Phycomp Vishay	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK ERJ8RQF1R0 V RC0805FR-0720K CRCW08050000Z0
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A R6, R6A, R6B, R6C, R6D R7, R9 R8, R13 R10, R38	PCB BS\$126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1% Resistor 1R0/200 V/1206/1% Resistor 20k/150 V/0805/1% Resistor 1.0k/150 V/0805/1%	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay Panasonic Yageo/Phycomp Vishay Bourns	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK ERJ8RQF1R0 V RC0805FR-0720K CRCW08050000Z0 CR0805-FX-1001ELF
1 1 1 2 1 2 6	Q1A Q3 Q4 Q5 Q6, Q7 Q8 R1, R2 R3, R3A, R4, R4A, R5, R5A R6, R6A, R6B, R6C, R6D R7, R9 R8, R13	PCB BS\$126/PG-SOT-23-3-5 MMBT3904/SOT-23-3 Transistor IPD60R280PFS/PG-T0252-3 BCX56-16/SOT89 Transistor IPN60R360P7S/PG-SOT-223 BCX56-16/SOT-89 Resistor 1.5 M/200 V/1206/1% Resistor 18k/200 V/1206/1% Resistor 1R0/200 V/1206/1% Resistor 0 R/150 V/0805/1% Resistor 0 R/150 V/0805/	NXP Semiconductors Infineon NXP Infineon NXP Yageo/Phycomp Vishay Panasonic Yageo/Phycomp Vishay	MMBT3904,215 IPD60R280P7S BCX56-16 IPN60R360P7S BCX56-16 RC1206FR-071M5L CRCW120618K0FK ERJ8RQF1R0 V RC0805FR-0720K CRCW08050000Z0



1 percent dimming with wide LED voltage and an integrated LLC transformer

2	R15, R16	Resistor 510k/150 V/0805/1%	Vishay	CRCW0805510KFKEA
1	R17	Resistor 43k/150 V/0805/1%	Vishay	CRCW080543K0FK
3	R18, R19,	Resistor 1.5 M/200 V/1206/1%	Yageo/Phycomp	RC1206FR-071M5L
3	R20	Nesistor 1.3 M/200 V/1200/170	rageo/r nycomp	RC12001 N-071M3L
1	R21	Resistor 24.9k/150 V/0805/1%	Vishay	CRCW080524K9FKEA
1	R22	Resistor 3k/200 V/1206/1%	Vishay	CRCW12063K00FKEA
1	R24	Resistor 11k/75 V/0603/1%	Vishay	CRCW060311K0FKEA
1	R25	Resistor 240k/75 V/0603/1%	Vishay	CRCW0603240KFK
1	R26	Resistor 56k/150 V/0805/1%	Vishay	CRCW080556K0FK
1	R27	Resistor 3.3k/75 V/0603/1%	Vishay	CRCW06033K30FK
1	R28	Resistor 2k/75 V/0603/1%	Vishay	CRCW06032K00FK
1	R29	NTC 100k/0805/5%	Epcos	B57471V2104J62
1	R30	Resistor 10 R/150 V/0805/1%	Vishay	CRCW080510R0FKEA
2	R31, R32	Resistor 22 R/150 V/0805/1%	Vishay	CRCW080522R0FKEA
4	R34, R34A,	Resistor 1.2 R/200 V/1206/1%	Vishay	CRCW12061R20FK
	R34B, R34C	, , ,	,	
2	R35, R36	Resistor 47k/150 V/0805/1%	Vishay	CRCW080547K0FKEA
1	R37	Resistor 330 R/150 V/0805/1%	Vishay	CRCW0805330RFKEA
1	R39	Resistor 3.3k/150 V/0805/1%	Vishay	CRCW08053K30FKEA
1	R40	Resistor 10 R/200 V/1206/1%	Vishay	CRCW120610R0FKEA
2	R41, R45	Resistor 3.6k/150 V/0805/1%	Vishay	CRCW08053K60FKEA
1	R42	Resistor 10k/150 V/0805/1%	Vishay	CRCW080510K0FK
2	R43, R56	Resistor 2.2M/200 V/1206/1%	Vishay	CRCW12062M20FKEA
1	R44	Resistor 20k/150 V/0805/1%	Vishay	CRCW080520K0FKEA
1	R46	Resistor 2.2 M/200 V/1206/1%	Vishay	CRCW12062M20FKEA
1	R47	Resistor 360k/150 V/0805/1%	Vishay	CRCW0805360KFKEA
1	R48	Resistor 3.9 M/150 V/0805/1%	Vishay	CRCW08053M90FKEA
1	R49	Resistor 4.3k/150 V/0805/1%	Vishay	CRCW08054K30FK
3	R50, R51,	Resistor 0.15 R/675 mV/1206/1%	Bourns	CRL1206-FW-R150ELF
	R52	,,		
1	R53	Resistor 2.0k/150 V/0805/1%	Vishay	CRCW08052K00FKEA
1	R54	Resistor 150k/200 V/1206/1%	Vishay	CRCW1206150KFKEA
1	R55	Resistor 33k/150 V/0805/1%	Vishay	CRCW080533K0FKEA
1	R57	Resistor 110k/75 V/0603/1%	Vishay	CRCW0603110KFK
1	R59	Resistor 3.6k/75 V/0603/1%	Vishay	CRCW06033K60FK
1	R62	Resistor 330k/150 V/0805/1%	Vishay	CRCW0805330KFKEA
1	TR1	Transistor TRLEV3001/THT	Itacoil	TRLEV3001
1	VR1	10D561K/560 V/	Bourns	MOV-10D561K
		VARRR750W80L1300T500H1600B/10%		
1	VR2	TL431CDBZR/2.495 V/SOT-23-3/	Texas Instruments	TL431CDBZR
1	X1	WAGO_250-203/WAGO_250-203/	WAGO	250-203
0	C10A	NA/25 V/CAPPRD250W50D630H1220B/20%	Würth Elektronik	860010473011
0	C17	NA/630 V DC/1206/X7R/10%	TDK	C3216X7R2J102K115AA
0	C18	NA/630 V DC/1206/X7R/10%	TDK	C3216X7R2J102K115AA
0	C36	NA/1206/X7R/10%	Murata	GRM31BR72J222KW01L
0	C53	NA/50 V/0805/X7R/10%	TDK	C2012X7R1H104K085AA
0	D1	NA/100 V/SOD-123	Diodes	1N4148W-7-F
			Incorporated	
0	D2	NA/1000 V/DO-214AC (SMA)	Vishay	US1M-E3/61T
0	D2	NA/1000 V/DO-214AC (SMA)	•	US1M-E3/61T



1 percent dimming with wide LED voltage and an integrated LLC transformer

0	D3	NA/30 V/DO-214AB (SMC)	Vishay	S5J-E3/57T
0	R23	Resistor NA/200 V/1206/1%	Vishay	CRCW120610R0FK
0	R58	Resistor 33k/150 V/0805/1%	Vishay	CRCW080533K0FK
0	R60	NA/50 V/0603/1%	Yageo/Phycomp	RC0603FR-07K
0	R61	NA/75 V/0603/20 mΩ	Vishay	CRCW06030000Z0EA



1 percent dimming with wide LED voltage and an integrated LLC transformer Revision history

Revision history

Document version	Date of release	Description of changes
V 1.0	2021-08-30	First release

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2021-08-30
Published by
Infineon AG
81726 Munich, Germany

© 2021 Infineon AG. All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference ER_2104_PL39_2104_123217

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon office.

Except as otherwise explicitly approved by Infineon in a written document signed by authorized representatives of Infineon, Infineon' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.

单击下面可查看定价,库存,交付和生命周期等信息

>>Infineon(英飞凌)